

## Introduction

This application note describes the design of a 6 channel power lines sequencer. It can be used for switching supply rails on/off in a predetermined order with constant or variable delays.

## Power Lines Sequencer circuit design

To design this sequencer it is necessary to construct a generator which sets the delay time, and DFFs and LUTs are used to shift the signal edges. Using blocks combinations “3-bit LUT + DFF” (cells) it is possible to sequence as many lines as the number of cells you have available. Cell configuration is shown in Figure 2, where N-1 = previous cell, N+1 = next cell.

The Generator block is made using 4-bit LUT0, CNT1/DLY1, 2-bit LUT1 and P DLY.

Blocks configurations are presented in figures 1-9.

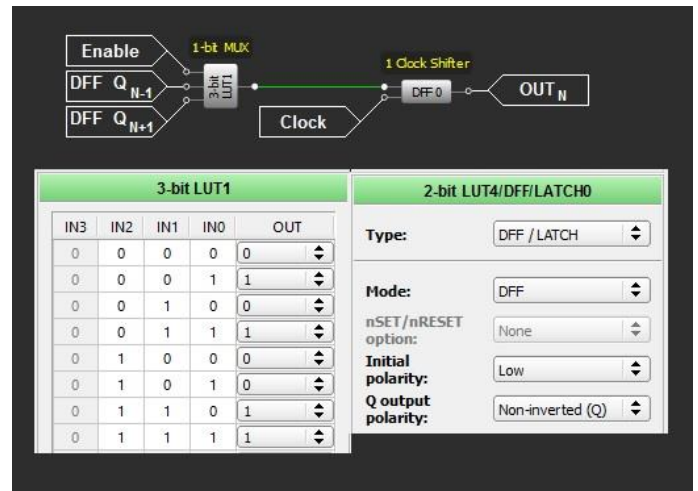


Figure 2. 3-bit LUT + DFF “cell” connections and configuration

 


Figure 3. P DLY configuration

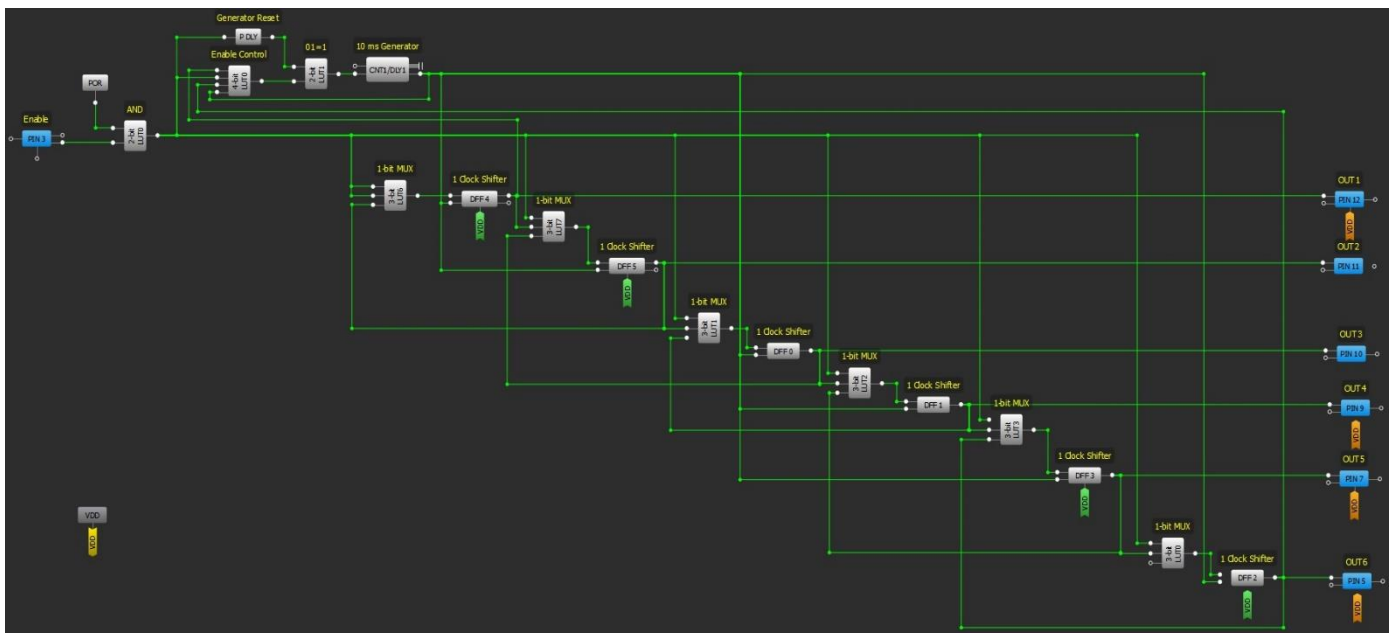


Figure 1. Power Lines Sequencer schematic



| PIN 3                  |                       |
|------------------------|-----------------------|
| I/O selection:         | Digital input         |
| Input mode:<br>OE = 0  | Digital in without Sc |
| Output mode:<br>OE = 1 | None                  |
| Resistor:              | Floating              |
| Resistor value:        | Floating              |
| PIN 5                  |                       |
| I/O selection:         | Digital output        |
| Input mode:<br>OE = 0  | None                  |
| Output mode:<br>OE = 1 | 1x push pull          |
| Resistor:              | Floating              |
| Resistor value:        | Floating              |
| PIN 7                  |                       |
| I/O selection:         | Digital output        |
| Input mode:<br>OE = 0  | None                  |
| Output mode:<br>OE = 1 | 1x push pull          |
| Resistor:              | Floating              |
| Resistor value:        | Floating              |
| PIN 9                  |                       |
| I/O selection:         | Digital output        |
| Input mode:<br>OE = 0  | None                  |
| Output mode:<br>OE = 1 | 1x push pull          |
| Resistor:              | Floating              |
| Resistor value:        | Floating              |
| PIN 10                 |                       |
| I/O selection:         | Digital output        |
| Input mode:<br>OE = 0  | None                  |
| Output mode:<br>OE = 1 | 1x push pull          |
| Resistor:              | Floating              |
| Resistor value:        | Floating              |
| PIN 11                 |                       |
| I/O selection:         | Digital output        |
| Input mode:<br>OE = 0  | None                  |
| Output mode:<br>OE = 1 | 1x push pull          |
| Resistor:              | Floating              |
| Resistor value:        | Floating              |
| PIN 12                 |                       |
| I/O selection:         | Digital output        |
| Input mode:<br>OE = 0  | None                  |
| Output mode:<br>OE = 1 | 1x push pull          |
| Resistor:              | Floating              |
| Resistor value:        | Floating              |

Figure 4. PINs configuration

| 2-bit LUT0 |     |     |     |     |   |
|------------|-----|-----|-----|-----|---|
| IN3        | IN2 | IN1 | IN0 | OUT |   |
| 0          | 0   | 0   | 0   | 0   | ↕ |
| 0          | 0   | 0   | 1   | 0   | ↕ |
| 0          | 0   | 1   | 0   | 0   | ↕ |
| 0          | 0   | 1   | 1   | 1   | ↕ |

| 4-bit LUT0/PGEN |     |     |     |     |   |
|-----------------|-----|-----|-----|-----|---|
| Type: LUT       |     |     |     |     |   |
| IN3             | IN2 | IN1 | IN0 | OUT |   |
| 0               | 0   | 0   | 0   | 0   | ↕ |
| 0               | 0   | 0   | 1   | 0   | ↕ |
| 0               | 0   | 1   | 0   | 0   | ↕ |
| 0               | 0   | 1   | 1   | 0   | ↕ |
| 0               | 1   | 0   | 0   | 1   | ↕ |
| 0               | 1   | 0   | 1   | 0   | ↕ |
| 0               | 1   | 1   | 0   | 0   | ↕ |
| 0               | 1   | 1   | 1   | 0   | ↕ |
| 1               | 0   | 0   | 0   | 1   | ↕ |
| 1               | 0   | 0   | 1   | 0   | ↕ |
| 1               | 0   | 1   | 0   | 1   | ↕ |
| 1               | 0   | 1   | 1   | 0   | ↕ |
| 1               | 1   | 0   | 0   | 1   | ↕ |
| 1               | 1   | 0   | 1   | 0   | ↕ |
| 1               | 1   | 1   | 0   | 0   | ↕ |
| 1               | 1   | 1   | 1   | 0   | ↕ |

| 2-bit LUT1 |     |     |     |     |   |
|------------|-----|-----|-----|-----|---|
| IN3        | IN2 | IN1 | IN0 | OUT |   |
| 0          | 0   | 0   | 0   | 0   | ↕ |
| 0          | 0   | 0   | 1   | 1   | ↕ |
| 0          | 0   | 1   | 0   | 0   | ↕ |
| 0          | 0   | 1   | 1   | 0   | ↕ |

| 3-bit LUT6/Pipe Delay |     |     |     |     |   |
|-----------------------|-----|-----|-----|-----|---|
| Type: LUT             |     |     |     |     |   |
| IN3                   | IN2 | IN1 | IN0 | OUT |   |
| 0                     | 0   | 0   | 0   | 0   | ↕ |
| 0                     | 0   | 0   | 1   | 1   | ↕ |
| 0                     | 0   | 1   | 0   | 0   | ↕ |
| 0                     | 0   | 1   | 1   | 1   | ↕ |
| 0                     | 1   | 0   | 0   | 0   | ↕ |
| 0                     | 1   | 0   | 1   | 0   | ↕ |
| 0                     | 1   | 1   | 0   | 1   | ↕ |
| 0                     | 1   | 1   | 1   | 1   | ↕ |

| 3-bit LUT7/8-bit CNT3/DLY3/FSM1 |     |     |     |     |   |
|---------------------------------|-----|-----|-----|-----|---|
| Type: LUT                       |     |     |     |     |   |
| IN3                             | IN2 | IN1 | IN0 | OUT |   |
| 0                               | 0   | 0   | 0   | 0   | ↕ |
| 0                               | 0   | 0   | 1   | 1   | ↕ |
| 0                               | 0   | 1   | 0   | 0   | ↕ |
| 0                               | 0   | 1   | 1   | 1   | ↕ |
| 0                               | 1   | 0   | 0   | 0   | ↕ |
| 0                               | 1   | 0   | 1   | 0   | ↕ |
| 0                               | 1   | 1   | 0   | 1   | ↕ |
| 0                               | 1   | 1   | 1   | 1   | ↕ |

Figure 5. LUTs configuration



| 3-bit LUT1 |     |     |     |     |
|------------|-----|-----|-----|-----|
| IN3        | IN2 | IN1 | IN0 | OUT |
| 0          | 0   | 0   | 0   | 0   |
| 0          | 0   | 0   | 1   | 1   |
| 0          | 0   | 1   | 0   | 0   |
| 0          | 0   | 1   | 1   | 1   |
| 0          | 1   | 0   | 0   | 0   |
| 0          | 1   | 0   | 1   | 0   |
| 0          | 1   | 1   | 0   | 1   |
| 0          | 1   | 1   | 1   | 1   |

| 3-bit LUT2 |     |     |     |     |
|------------|-----|-----|-----|-----|
| IN3        | IN2 | IN1 | IN0 | OUT |
| 0          | 0   | 0   | 0   | 0   |
| 0          | 0   | 0   | 1   | 1   |
| 0          | 0   | 1   | 0   | 0   |
| 0          | 0   | 1   | 1   | 1   |
| 0          | 1   | 0   | 0   | 0   |
| 0          | 1   | 0   | 1   | 0   |
| 0          | 1   | 1   | 0   | 1   |
| 0          | 1   | 1   | 1   | 1   |

| 3-bit LUT3 |     |     |     |     |
|------------|-----|-----|-----|-----|
| IN3        | IN2 | IN1 | IN0 | OUT |
| 0          | 0   | 0   | 0   | 0   |
| 0          | 0   | 0   | 1   | 1   |
| 0          | 0   | 1   | 0   | 0   |
| 0          | 0   | 1   | 1   | 1   |
| 0          | 1   | 0   | 0   | 0   |
| 0          | 1   | 0   | 1   | 0   |
| 0          | 1   | 1   | 0   | 1   |
| 0          | 1   | 1   | 1   | 1   |

| 3-bit LUT0 |     |     |     |     |
|------------|-----|-----|-----|-----|
| IN3        | IN2 | IN1 | IN0 | OUT |
| 0          | 0   | 0   | 0   | 0   |
| 0          | 0   | 0   | 1   | 1   |
| 0          | 0   | 1   | 0   | 0   |
| 0          | 0   | 1   | 1   | 1   |
| 0          | 1   | 0   | 0   | 0   |
| 0          | 1   | 0   | 1   | 0   |
| 0          | 1   | 1   | 0   | 1   |
| 0          | 1   | 1   | 1   | 1   |

Figure 6. LUTs configuration

| DFF/LATCH4          |                  |
|---------------------|------------------|
| Mode:               | DFF              |
| nSET/nRESET option: | nRESET           |
| Initial polarity:   | Low              |
| Q output polarity:  | Non-inverted (Q) |

| DFF/LATCH5          |                  |
|---------------------|------------------|
| Mode:               | DFF              |
| nSET/nRESET option: | nRESET           |
| Initial polarity:   | Low              |
| Q output polarity:  | Non-inverted (Q) |

| 2-bit LUT4/DFF/LATCH0 |                  |
|-----------------------|------------------|
| Type:                 | DFF / LATCH      |
| Mode:                 | DFF              |
| nSET/nRESET option:   | None             |
| Initial polarity:     | Low              |
| Q output polarity:    | Non-inverted (Q) |

| 2-bit LUT5/DFF/LATCH1 |                  |
|-----------------------|------------------|
| Type:                 | DFF / LATCH      |
| Mode:                 | DFF              |
| nSET/nRESET option:   | None             |
| Initial polarity:     | Low              |
| Q output polarity:    | Non-inverted (Q) |

| 3-bit LUT5/DFF/LATCH3 |                  |
|-----------------------|------------------|
| Type:                 | DFF / LATCH      |
| Mode:                 | DFF              |
| nSET/nRESET option:   | nRESET           |
| Initial polarity:     | Low              |
| Q output polarity:    | Non-inverted (Q) |

| 3-bit LUT4/DFF/LATCH2 |                  |
|-----------------------|------------------|
| Type:                 | DFF / LATCH      |
| Mode:                 | DFF              |
| nSET/nRESET option:   | nRESET           |
| Initial polarity:     | Low              |
| Q output polarity:    | Non-inverted (Q) |

Figure 7. DFFs configuration

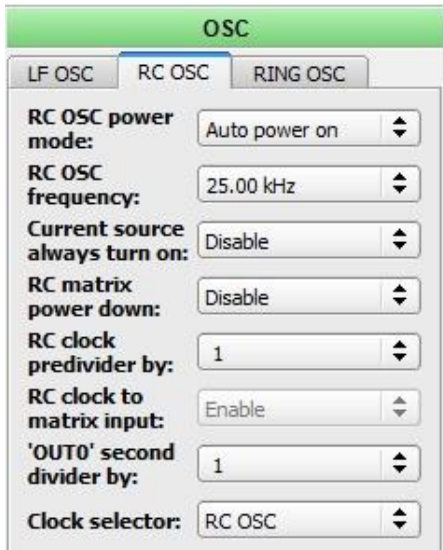


Figure 8. ADC properties

 


Figure 9. DLY1 configuration

### Power Lines Sequencer circuit analysis

As we know, a DFF can shift an input signal (D input) by 1 clock. The point is to form this input signal using existing signals (Enable, Previous line, Next line), which are applied to 3-bit LUT.

This 3-bit LUT operates as a MUX and outputs N-1 signal when Enable is HIGH, and N+1 signal when Enable is LOW (see figure 10).

4-bit LUT0 is used to turn on/off the generator when it is necessary to decrease current consumption. Its output will invert the IN0 input signal until the lines are all HIGH or all LOW (see figure 10). 2-bit LUT1 repeats the 4-bit LUT0 value when P DLY output is LOW. When the pulse comes from PDLY block, 2-bit LUT1 output goes LOW. This will reset the generator on the rising or falling edge of Enable signal, and that provides proper delay for the last (6<sup>th</sup>) line's falling edge (figure 11).

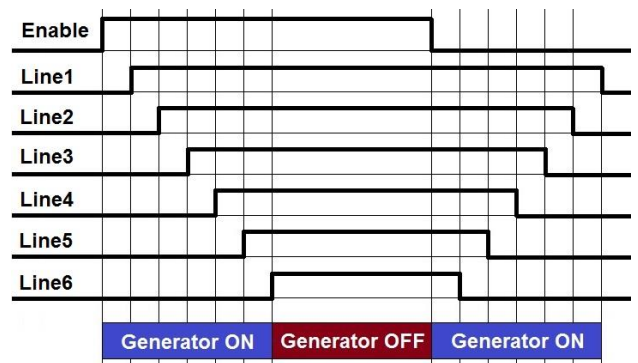


Figure 10. Power Lines Sequencer theoretical timing diagram

 


Figure 11. Power Lines Sequencer Scope Shot D0 – Enable; D1 – Line1; D2 – Line2; D3 – Line3; D4 – Line4; D5 – Line5; D6 – Line6.

 


Figure 12. Power Lines Sequencer Scope Shot  
D0 – Enable; D1 – Line1; D2 – Line2; D3 – Line3;  
D4 – Line4; D5 – Line5; D6 – Line6.

 


Figure 13. Power Lines Sequencer theoretical timing diagram  
D0 – Enable; D1 – Line1; D2 – Line2; D3 – Line3;  
D4 – Line4; D5 – Line5; D6 – Line6.

In the case when Enable goes low before some lines are driven high, these lines will stay LOW (see figure 12).

In the case Enable signal comes before some lines are driven LOW, these lines will stay HIGH (see figure 13).

No additional blocks are required to provide these functions. It is realized only with 3-bit LUTs and DFFs, described earlier.

Also it is possible to make a circuit simplification (Figure 14). That can be done for the first and last 3-bit LUT + DFF cells. In the first case, Enable signal and “Previous line” have the same timing. So 3-bit LUT can be replaced with a 2-bit LUT, configured as an OR gate (see figure 15).

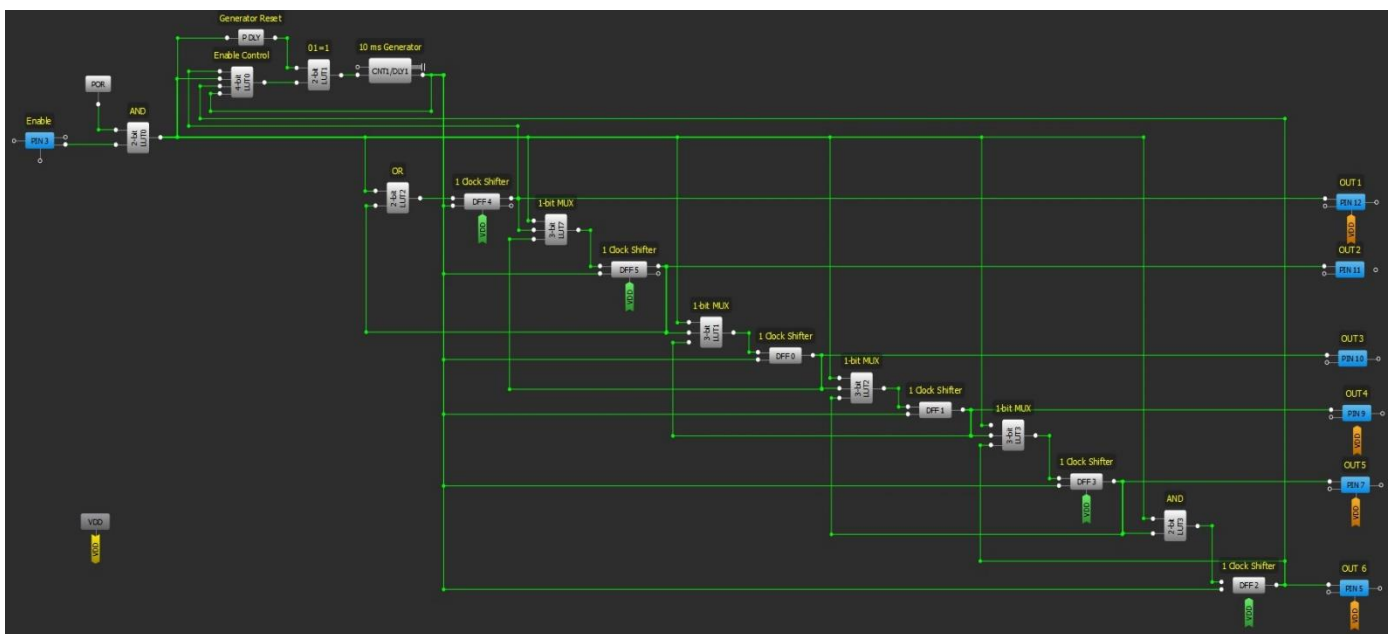


Figure 14. Simplified Power Lines Sequencer circuit design



As for the last line, there is no Next line and one of the 3-bit LUT's inputs stays LOW all the time. This LUT can be replaced with a 2-bit LUT (AND gate) as well (figure 15).

## Power Lines Sequencer with variable delay time

Using a state machine instead of a simple Delay block makes it possible to change a delay time by loading counter data from the ADC. The Power lines sequencer with variable delay time circuit is presented in figure 17.

Configuration of the LUT + DFF cells remains the same, but there are some changes in the generator operation process and some blocks are added (see figure 17). The corresponding Blocks configuration is shown in figures 18-22.

| 2-bit LUT2 |     |     |     |     |
|------------|-----|-----|-----|-----|
| IN3        | IN2 | IN1 | IN0 | OUT |
| 0          | 0   | 0   | 0   | 0   |
| 0          | 0   | 0   | 1   | 1   |
| 0          | 0   | 1   | 0   | 1   |
| 0          | 0   | 1   | 1   | 1   |

| 2-bit LUT3 |     |     |     |     |
|------------|-----|-----|-----|-----|
| IN3        | IN2 | IN1 | IN0 | OUT |
| 0          | 0   | 0   | 0   | 0   |
| 0          | 0   | 0   | 1   | 0   |
| 0          | 0   | 1   | 0   | 0   |
| 0          | 0   | 1   | 1   | 1   |

Figure 15. 2-bit LUTs configuration

| PIN 6                  |                     |
|------------------------|---------------------|
| I/O selection:         | Analog input/output |
| Input mode:<br>OE = 0  | Analog input        |
| Output mode:<br>OE = 1 | Analog output       |
| Resistor:              | Floating            |
| Resistor value:        | Floating            |

Figure 16. PIN6 properties

 


Figure 17. Schematic of Power Lines Sequencer with variable delay time



| ADC                           |                                    |
|-------------------------------|------------------------------------|
| Mode:                         | Single-end                         |
| Vref:                         | Bandgap (1 V)                      |
| Force analog part:            | Disable                            |
| Analog part speed selection:  | 5 kHz                              |
| Clock for ADC divide by:      | 1                                  |
| ADC data sync with SPI clock: | Disable                            |
| PWM & ADC clock source :      | RC OSC                             |
| Sample speed:                 | 97.6562 Hz <a href="#">Formula</a> |
| Connections                   |                                    |
| Serial data:                  | Disable (Matrix <->)               |

Figure 19. ADC properties

| DCMP0/PWM0                     |            |
|--------------------------------|------------|
| DCMP/PWM power register:       | Power on   |
| Function selection:            | DCMP       |
| PD sync to clock:              | Off        |
| Clock source:                  | ADC CLK    |
| Clock invert:                  | Disable    |
| PWM & ADC clock source :       | RC OSC     |
| PWM data sync with SPI clock:  | Disable    |
| Duty cycle:                    | 0% - 99.6% |
| PWM deadband time:             | 10 ns      |
| Register 0:<br>MTRX SEL: (0:0) | 0          |
| Register 1:<br>MTRX SEL: (0:1) | 0          |
| Register 2:<br>MTRX SEL: (1:0) | 0          |
| Register 3:<br>MTRX SEL: (1:1) | 0          |
| Connections                    |            |
| IN+ selector:                  | ADC [7:0]  |
| IN- selector:                  | Register 0 |

Figure 20. DCMP properties

| PGA               |            |
|-------------------|------------|
| Power on signal:  | Power down |
| Gain:             | x1         |
| ADC mode:         | Single-end |
| Connections       |            |
| Channel selector: | VDD        |
| IN+ Channel 1:    | PIN 6      |
| IN+ Channel 2:    | None       |
| IN- Channel:      | None       |
| External output:  | Disable    |

Figure 18. PGA properties



WS Ctrl/14-bit CNT0/DLY0

Type:

Mode:

Counter data:   
(Range: 1 - 16383)

Delay time: 1.3000 ms [Formula](#)

Edge select:

Q mode:

DFF bypass enable:

Connections

FSM data:

Clock:

Clock source: OSC Freq.

4-bit LUT1/14-bit CNT2/DLY2/FSM0

Type:

Mode:

Counter data:   
(Range: 1 - 16383)

Delay time: 0.1400 ms [Formula](#)

Edge select:

Q Mode:

FSM data sync with SPI clock:

Connections

FSM data:

Clock:

Clock source: OSC Freq.

Figure 21. DLYs properties

4-bit LUT0/PGEN

Type:

| IN3 | IN2 | IN1 | IN0 | OUT |
|-----|-----|-----|-----|-----|
| 0   | 0   | 0   | 0   | 0   |
| 0   | 0   | 0   | 1   | 1   |
| 0   | 0   | 1   | 0   | 0   |
| 0   | 0   | 1   | 1   | 1   |
| 0   | 1   | 0   | 0   | 0   |
| 0   | 1   | 0   | 1   | 0   |
| 0   | 1   | 1   | 0   | 1   |
| 0   | 1   | 1   | 1   | 1   |
| 1   | 0   | 0   | 0   | 0   |
| 1   | 0   | 0   | 1   | 0   |
| 1   | 0   | 1   | 0   | 0   |
| 1   | 0   | 1   | 1   | 0   |
| 1   | 1   | 0   | 0   | 0   |
| 1   | 1   | 0   | 1   | 0   |
| 1   | 1   | 1   | 0   | 0   |
| 1   | 1   | 1   | 1   | 0   |

3-bit LUT0

| IN3 | IN2 | IN1 | IN0 | OUT |
|-----|-----|-----|-----|-----|
| 0   | 0   | 0   | 0   | 1   |
| 0   | 0   | 0   | 1   | 0   |
| 0   | 0   | 1   | 0   | 0   |
| 0   | 0   | 1   | 1   | 0   |
| 0   | 1   | 0   | 0   | 0   |
| 0   | 1   | 0   | 1   | 0   |
| 0   | 1   | 1   | 0   | 0   |
| 0   | 1   | 1   | 1   | 0   |
| 1   | 0   | 0   | 0   | 0   |

3-bit LUT6/Pipe Delay

Type:

| IN3 | IN2 | IN1 | IN0 | OUT |
|-----|-----|-----|-----|-----|
| 0   | 0   | 0   | 0   | 1   |
| 0   | 0   | 0   | 1   | 0   |
| 0   | 0   | 1   | 0   | 0   |
| 0   | 0   | 1   | 1   | 0   |
| 0   | 1   | 0   | 0   | 0   |
| 0   | 1   | 0   | 1   | 0   |
| 0   | 1   | 1   | 0   | 0   |
| 0   | 1   | 1   | 1   | 1   |

Figure 22. LUTs properties






An analog voltage comes from PIN6, configured as analog input, to the PGA and then – to ADC block, which converts it into 8-bit code. Then this code can be loaded into CNT2/DLY2/FSM0 block as counter data. So by the changing Pin6 analog input voltage, it is possible to change delay time between power lines switching. As in previous circuits, the generator operation time range is determined by LUT “Enable Control”, but for generator reset (by P DLY in both edge detector mode) 3-bit LUT0 is used. CNT0/DLY0 block is needed to switch generator on after the ADC outputs its first proper parallel data. When the ADC input voltage is less than ADC offset (about 50mV), the ADC will output 8-bit logic 0, which will make the generator not operational. To remedy this situation, DCMP checks if ADC data is equal to 0. If it is, a 1-bit MUX with Enable (4-bit LUT0) will output its signal (after CNT0/DLY0 delay) from the OSC (minimum delay time). If it is not equal to 0 – then signaling is from CNT2/DLY2/FSM0 + 3-bit LUT0 generator.

### Conclusion

Using only one SLG46140 chip it is possible to create a power lines sequencer for six (or even more) lines with constant or variable delay between lines switching. Current consumption is also optimized (at 3.3V VDD): 150uA during lines switching on/off (dynamic), and 0uA when lines are settled (static).

 

**Figure 23. Timing diagram of Power Lines Sequencer with variable delay**

CH1 – V-IN; D0 – Enable; D1 – Line1; D2 – Line2;  
D3 – Line3; D4 – Line4; D5 – Line5; D6 – Line6.



### About the Author

Name: Yurii Shchebel

Background: Yurii Shchebel graduated from Ivan Franko Lviv National University in 2015, studying at the Department Electronics. Presently he is working with Configurable Mixed Signal ICs (CMICs) and their applications. He has additional interests designing audiophile grade amplifiers.

Contact: [appnotes@silego.com](mailto:appnotes@silego.com)



### Document History

Document Title: Power Lines Sequencer

Document Number: AN-1074

| Revision | Orig. of Change | Submission Date | Description of Change |
|----------|-----------------|-----------------|-----------------------|
| A        | Yurii Shchebel  | 6/11/2015       | New application note  |

### Worldwide Sales and Design Support

Silego Technology maintains a worldwide network of offices, solution centers, manufacturer's representatives, and distributors. To find the office closest to you, visit us at [Silego Locations](#).

### About Silego Technology

Silego Technology, Inc. is a fabless semiconductor company headquartered in Santa Clara, California, with operations in Taiwan, and additional design/technology centers in China, Korea and Ukraine.



**SILEGO**  
TECHNOLOGY

Silego Technology Inc.  
1515 Wyatt Drive  
Santa Clara, CA 95054

**Phone** : 408-327-8800  
**Fax** : 408-988-3800  
**Website** : [www.silego.com](http://www.silego.com)